
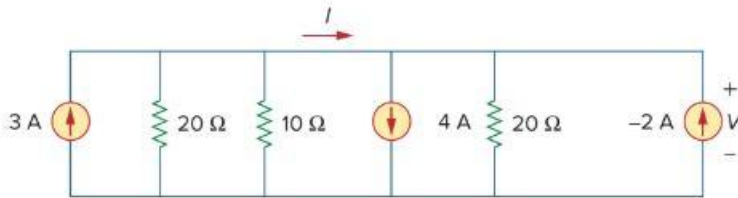


Homework 2

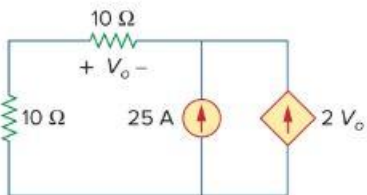
2.18 Find I and V in the circuit of Fig. 2.82.




2.22 Find V_o in the circuit in Fig. 2.86 and the power absorbed by the dependent source.



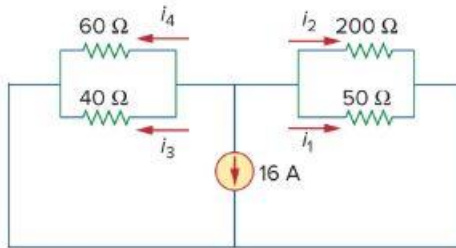
2.32 Find i_1 through i_4 in the circuit in Fig. 2.96.



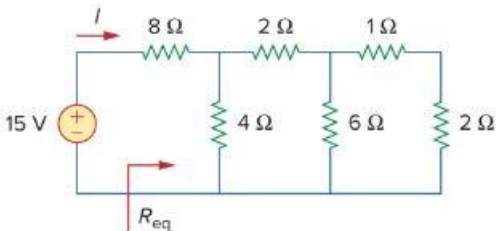2.40 For the ladder network in Fig. 2.104, find I and R_{eq} .



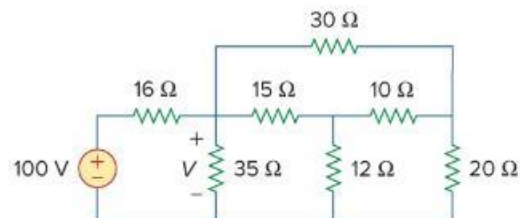2.56 Determine V in the circuit of Fig. 2.120.



2.69 A voltmeter is used to measure V_o in the circuit in Fig. 2.129. The voltmeter model consists of an ideal voltmeter in parallel with a $250\text{-k}\Omega$ resistor. Let $V_s = 95\text{ V}$, $R_s = 25\text{ k}\Omega$ and $R_1 = 40\text{ k}\Omega$. Calculate V_o with and without the voltmeter when

(a) $R_2 = 5\text{ k}\Omega$

Answer

(b) $R_2 = 25\text{ k}\Omega$

Answer

(c) $R_2 = 250\text{ k}\Omega$

Answer

